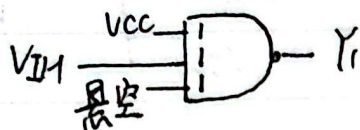


23376275 何宗霖


VLSI - 第三周作业.

1. ①




$$Y_1 = \overline{1 \cdot 1 \cdot 1} = 0.$$

②

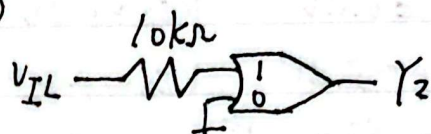


$$Y_2 = 1 + 0 = 1$$

③

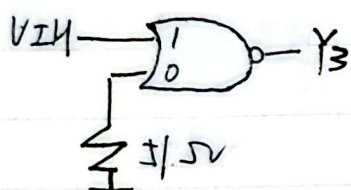


$$Y_3 = \overline{1 \cdot 0} = 1$$

④

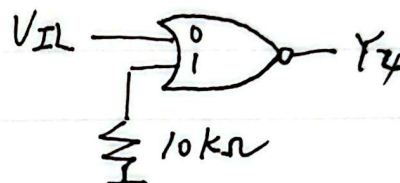


$$Y_4 = \overline{0 + 1} = 0.$$

⑤

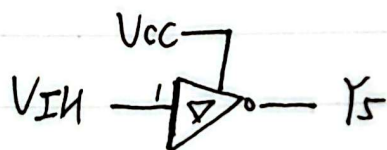


$$Y_5 = \overline{1} = 0.$$

⑥

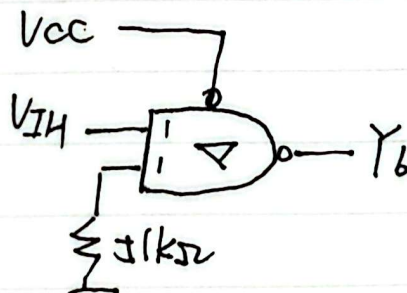Y₆: 高阻态


⑦

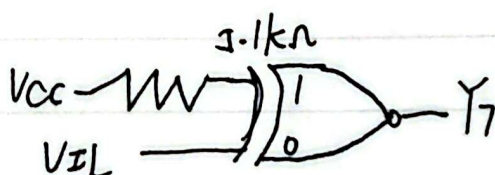

~~$$Y_7 = \overline{1 \cdot 0 + 1 \cdot 0} = 1$$~~

$$Y_7 = 1 \cdot 0 + 1 \cdot 0 = 0$$

⑧

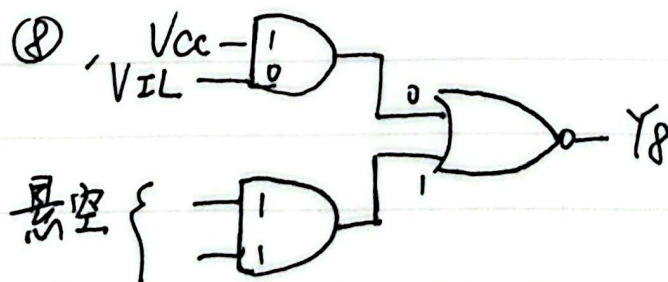

$$Y_8 = \overline{1 \cdot 0 + 1 \cdot 1} = 0.$$

2. (1) V_{I1} 悬空 $V_{I2} = 1.4V$
 (2) $V_{I1} = 0.2V$ $V_{I2} = 0.2V$
 (3) $V_{I1} = 3.2V$ $V_{I2} = 1.4V$
 (4). V_{I1} 经 $5k\Omega$ 接地 $V_{I2} = 0V$
 (5). V_{I1} 经 $10k\Omega$ 接地 $V_{I2} = 1.4V$

