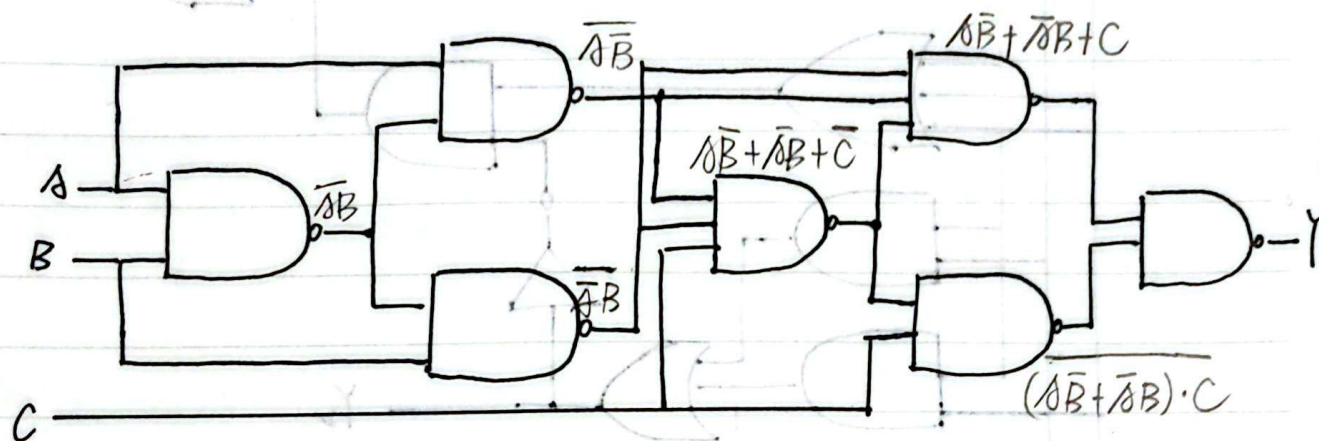


23376275 - 何宗霖

VLSI - 第7周作业.

1. (1)



$$\overline{A\bar{B}} \cdot \overline{\bar{A}B} \cdot C = A\bar{B} + \bar{A}B + \bar{C}$$

$$\overline{A\bar{B}} \cdot \overline{\bar{A}B} \cdot (A\bar{B} + \bar{A}B + \bar{C}) = A\bar{B} + \bar{A}B + C$$


$$\therefore Y = (A\bar{B} + \bar{A}B + C) \cdot (A\bar{B} + \bar{A}B) \cdot C = \overline{A\bar{B} + \bar{A}B} \cdot \bar{C} + (A\bar{B} + \bar{A}B) \cdot C$$

$$= (A \oplus B) \odot C$$

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

[注].  $(A \oplus B) \odot C = (A \odot B) \oplus C$

功能: 判断 ABC 是否有偶数个 1.

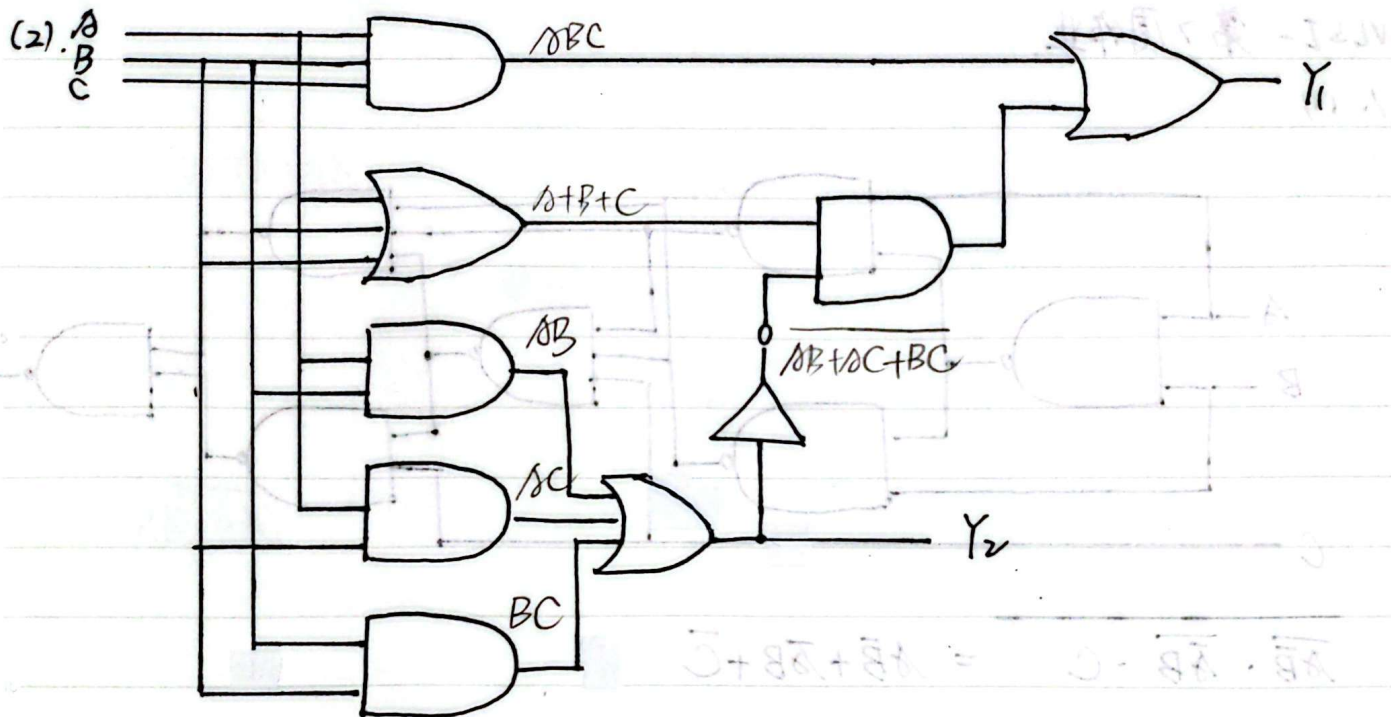

$$Y_1 = A \oplus B \oplus C$$

$$Y_2 = AB + AC + BC$$

| A | B | C | $Y_1$ | $Y_2$ |
|---|---|---|-------|-------|
| 0 | 0 | 0 | 0     | 0     |
| 0 | 0 | 1 | 1     | 0     |
| 0 | 1 | 0 | 1     | 0     |
| 1 | 0 | 0 | 1     | 0     |
| 0 | 1 | 1 | 0     | 1     |
| 1 | 0 | 1 | 0     | 1     |
| 1 | 1 | 0 | 0     | 1     |
| 1 | 1 | 1 | 1     | 1     |

功能:  $Y_1$  为全加器 2 个一位全加器所本位

$Y_2$  为 2 个一位全加器所进位。

2. 由图可知

$$Y = \overline{A}BS_1 \cdot \overline{A'}BS_1 \cdot \overline{A}B'S_2 \cdot \overline{A'}B'S_3$$

| $S_0$ | $S_1$ | $S_2$ | $S_3$ | $Y$                             |
|-------|-------|-------|-------|---------------------------------|
| 0     | 0     | 0     | 0     | 1                               |
| 0     | 0     | 0     | 1     | $A+B$                           |
| 0     | 0     | 1     | 0     | $\overline{A}+B$                |
| 0     | 1     | 0     | 0     | $A+\overline{B}$                |
| 1     | 0     | 0     | 0     | $\overline{A}+\overline{B}$     |
| 0     | 0     | 1     | 1     | $B$                             |
| 0     | 1     | 0     | 1     | $A$                             |
| 1     | 0     | 0     | 1     | $A \oplus B$                    |
| 0     | 1     | 1     | 0     | $AB + \overline{A}\overline{B}$ |
| 1     | 0     | 1     | 0     | $\overline{A}$                  |
| 1     | 1     | 0     | 0     | $\overline{B}$                  |
| 0     | 1     | 1     | 1     | $AB$                            |
| 1     | 0     | 1     | 1     | $\overline{A}B$                 |
| 1     | 1     | 0     | 1     | $A\overline{B}$                 |
| 1     | 1     | 1     | 0     | $\overline{A}\overline{B}$      |
| 1     | 1     | 1     | 1     | 0                               |



7. 列出真值表

| A | B | C | $M_s$ | $M_L$ |
|---|---|---|-------|-------|
| 0 | 0 | 0 | 0     | 0     |
| 0 | 0 | 1 | 1     | 0     |
| 0 | 1 | 0 | X     | X     |
| 1 | 0 | 0 | X     | X     |
| 0 | 1 | 1 | 0     | 1     |
| 1 | 0 | 1 | X     | X     |
| 1 | 1 | 0 | X     | X     |
| 1 | 1 | 1 | 1     | 1     |

(打X表示非法输入)

对于  $M_s$


| $C \backslash AB$ | 00 | 01 | 11 | 10 |
|-------------------|----|----|----|----|
| 1                 | 1  | 0  | 1  | X  |
| 0                 | 0  | X  | X  | X  |

对于  $M_L$

| $C \backslash AB$ | 00 | 01 | 11 | 10 |
|-------------------|----|----|----|----|
| 1                 | 0  | 1  | 1  | X  |
| 0                 | 0  | X  | X  | X  |

$$\text{令 } M_s = \overline{A} \overline{B} C + A B C = (\overline{A} \oplus B) \cdot C$$

$$M_L = B$$

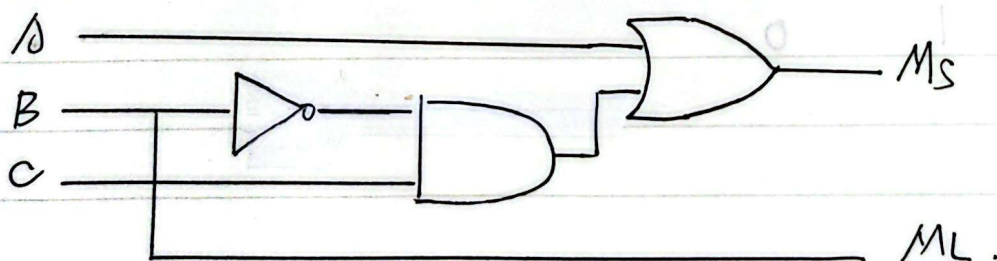

$$4. Y_1 = AC = ABC + A\bar{B}C = \bar{7}'' + \bar{5}''$$

$$Y_2 = A'B'C + ABC' + BC = A'B'C + AB'C' + A'BC + ABC = \bar{1}'' + \bar{4}'' + \bar{3}'' + \bar{7}''$$

$$Y_3 = B'C' + ABC' = A'B'C' + AB'C' + ABC' = \bar{0}'' + \bar{4}'' + \bar{6}''$$

