
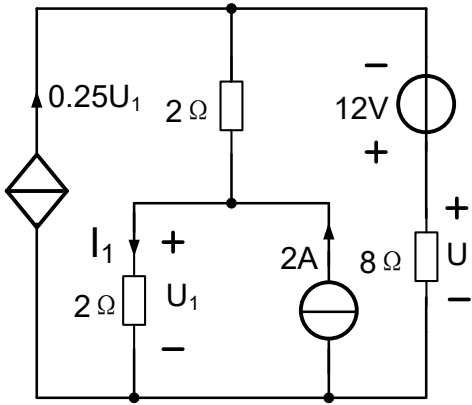



一、电路如下图所示，用戴维宁定理求电流求电压 U 。

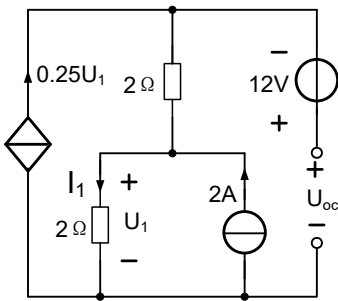


解：


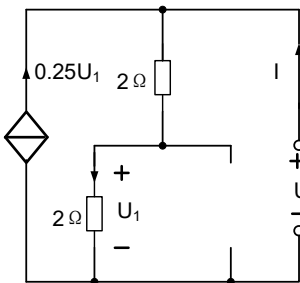
$$\begin{aligned} 0.25U_1 + 2 &= I_1 = 0.5U_1 \\ U_1 &= 8V \\ U_{oc} &= 2 \times 0.25U_1 + U_1 + 12 = 24V \end{aligned}$$


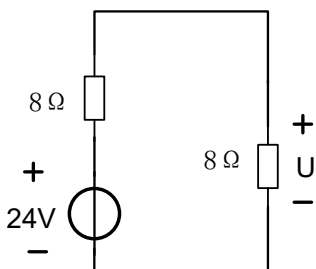
$$\begin{aligned} I + 0.25U_1 &= 0.25U \\ U_1 &= 0.5U \\ I &= 0.125U \\ R_0 &= \frac{U}{I} = 8\Omega \end{aligned}$$



$$U = 0.5 \times 24 = 12V$$